

Tutorial 4

ECE1388 Project 3

4x4 Array Multiplier

Mustafa Kanchwala
ECE1388

What is our target?

❑ Example:

1100	:	12_{10}	multiplicand
<u>0101</u>	:	5_{10}	multiplier

_____	:	60_{10}	product
-------	---	-----------	---------

❑ M x N-bit multiplication

General Form

❑ Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$

❑ Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

❑ Product: $P = \left(\sum_{j=0}^{M-1} \overset{Y}{y_j} 2^j \right) \left(\sum_{i=0}^{N-1} \overset{X}{x_i} 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$

						y_5	y_4	y_3	y_2	y_1	y_0	
						x_5	x_4	x_3	x_2	x_1	x_0	
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$				
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$					
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$						
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

multiplicand

multiplier

partial

products

product

Multiplication

□ Example:

1100	:	12_{10}	multiplicand
<u>0101</u>	:	5_{10}	multiplier
			partial products
<hr/>			product

- M x N-bit multiplication
- Produce N M-bit partial products
 - Sum these to produce M+N-bit product

Multiplication


❑ Example:

1100	:	12_{10}	multiplicand
<u>0101</u>	:	5_{10}	multiplier
			partial products
<hr/>			product

- ❑ M x N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product

Multiplication

□ Example:

 

□ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

Multiplication

□ Example:

$$\sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

$$\begin{array}{r} 1100 \\ 0101 \\ \hline 1100 \\ 0000 \end{array}$$

$$\begin{array}{l} 12_{10} \\ 5_{10} \\ \hline \end{array}$$

multiplicand

multiplier

partial products

product

$$\begin{array}{cccc} y_3 x_0 & y_2 x_0 & y_1 x_0 & y_1 x_0 \\ y_3 x_1 & y_2 x_1 & y_1 x_1 & y_1 x_1 \end{array}$$

□ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

Multiplication

❑ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline \end{array}$$

multiplicand
multiplier
partial products
product

❑ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

Multiplication

❑ Example:

1100	:	12_{10}	multiplicand
0101	:	5_{10}	multiplier
<hr/>			
1100] partial products
0000			
1100			
0000			
<hr/>			
			product

❑ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

Multiplication

❑ Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline \end{array}$$

multiplicand
multiplier
partial products
product

❑ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product


How do we perform multi-input addition?

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{\text{out}} = A \bullet B$$

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$




 


A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Carry Propagate Adders


□ N-bit adder called CPA

  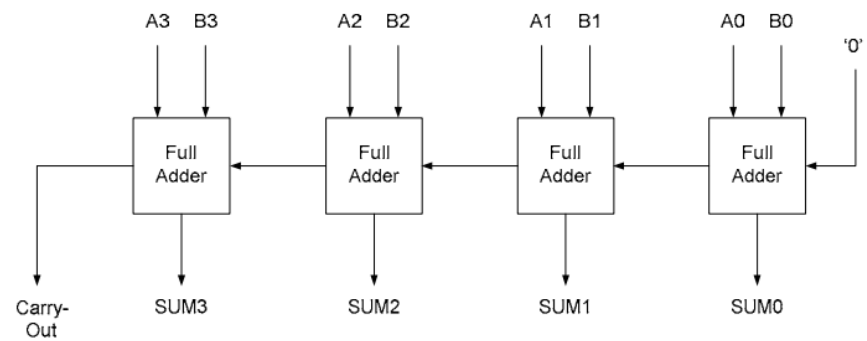 - Each sum bit depends on all previous carries
- How do we compute all these carries quickly?




Multi-input Adders

 - ❑ Suppose we want to add k N-bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- ❑ Straightforward solution: k-1 N-input CPAs
 - Large and slow




Carry Save Addition

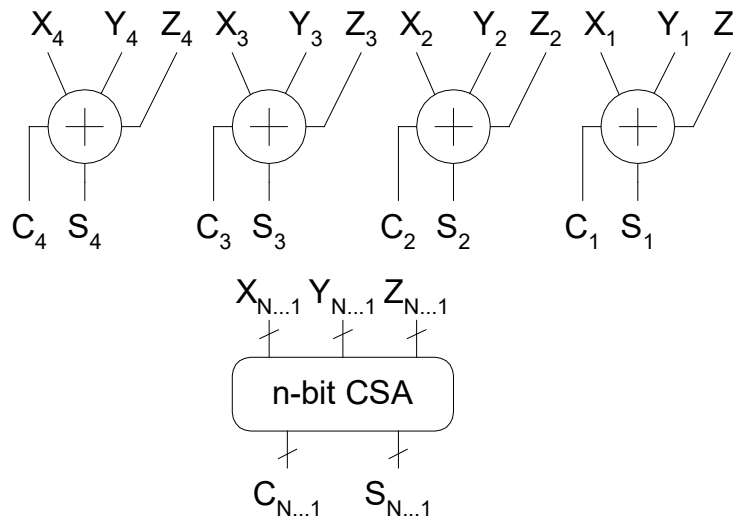- ❑ A full adder sums 3 inputs and produces 2 outputs
 - Carry output has twice *weight* of sum output
- ❑ N full adders in parallel are called *carry save adder*
 - Produce N sums and N carry outs



Array Multiplier

 


$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 00111100 : 60_{10}
 \end{array}$$

multiplicand
multiplier


partial
products

product

 

Design


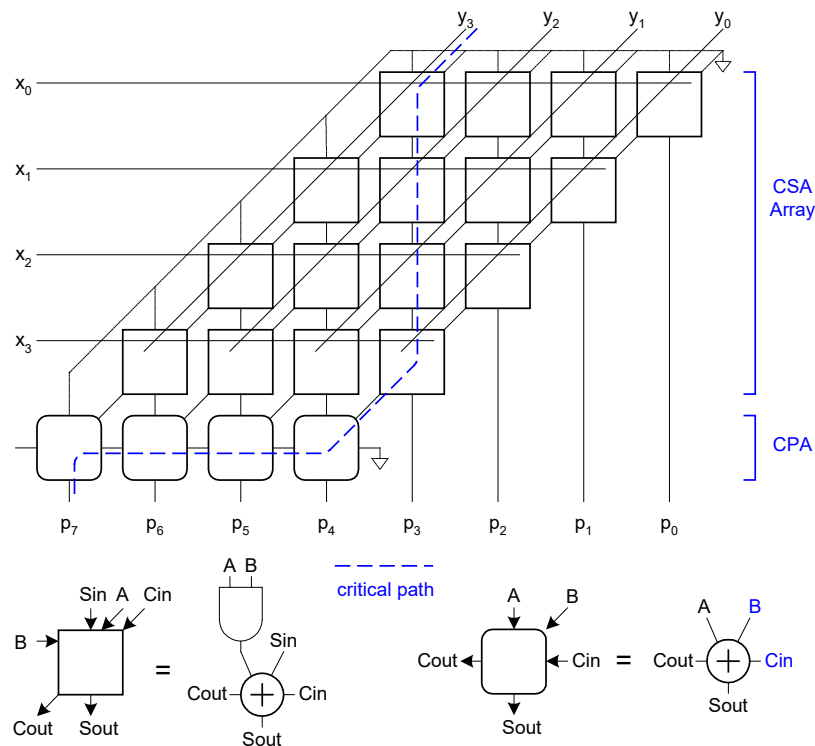
- Using Verilog, describe the digital logic of an unsigned array multiplier to calculate the unsigned product of two unsigned 4-bit numbers. Provide the full Verilog code in your report.




Simulation

- ❑ You have been provided with an exhaustive Verilog test bench to verify the functionality of your 4x4 multiplier.
- ❑ You can use NCVerilog (or Modelsim) to run the test bench with the following Linux command:
ncverilog multiplier.v testbench.v (for NCVerilog)
 - Follow guidance in VLSI User Manual for Modelsim simulation
- ❑ You must include `timescale 1ns/1ps before your multiplier module declaration.
- ❑ Provide the output of the test bench dialogue in your report to show the functionality of your multiplier.

Synthesis

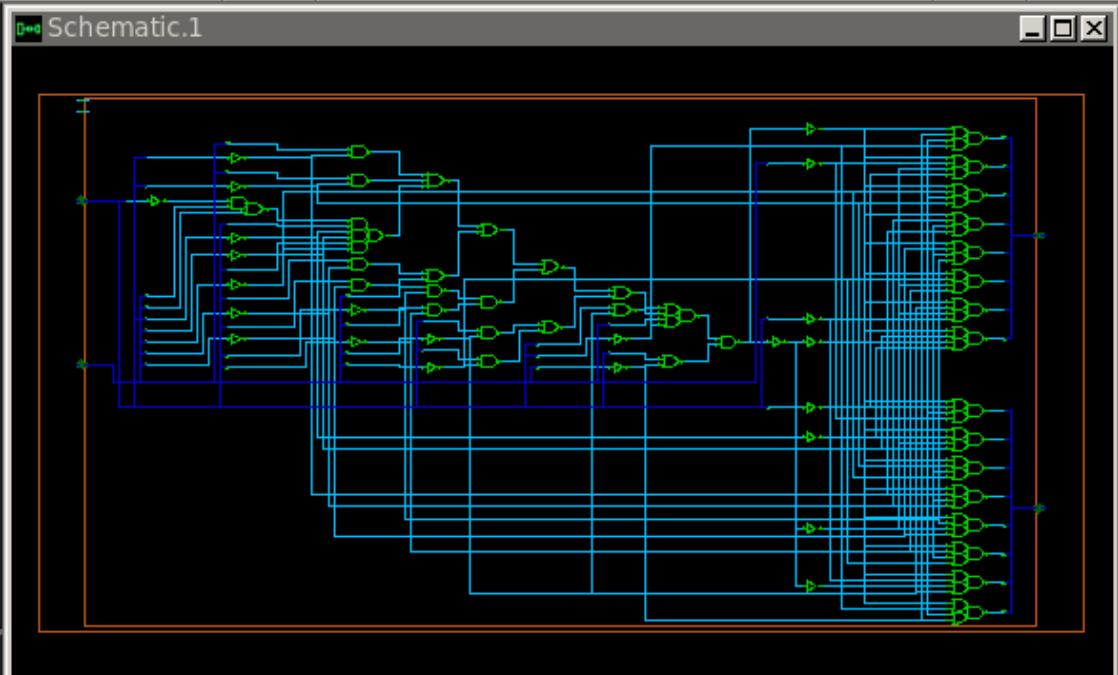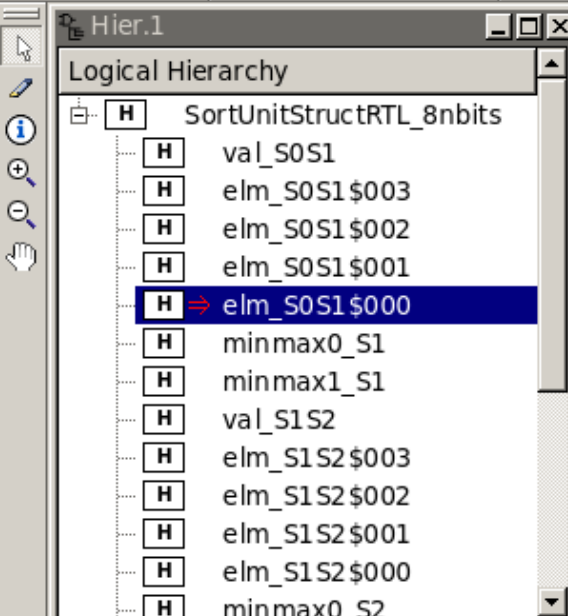

HistList.1 - HistList.1 Path S...

 


Worst

Best

0.00180304

0.00439787

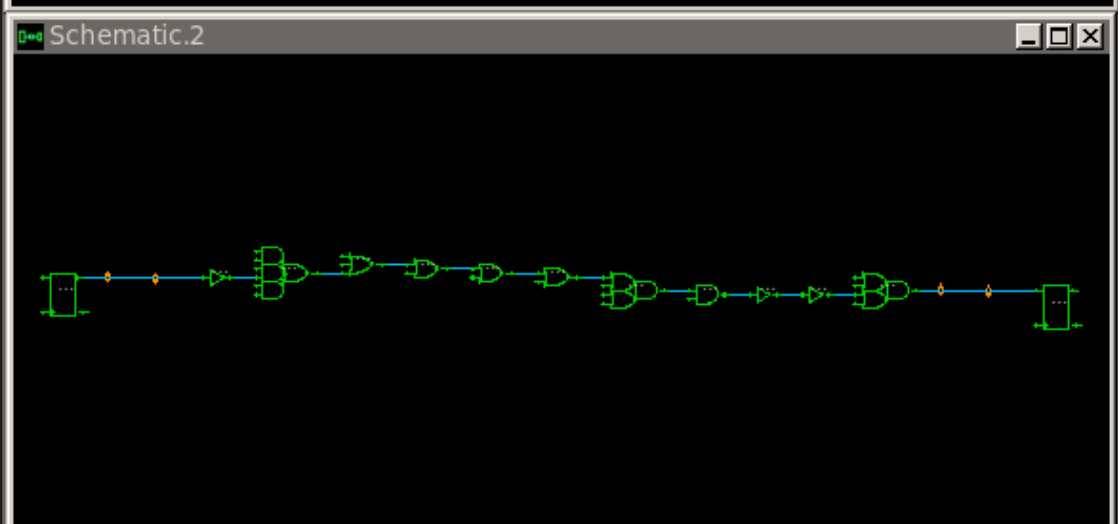

Hier.1



Schematic.1



HistList.1



Schematic.2

1

- ❑ Place the synthesis.tcl file in the same working directory as the Verilog test bench and your multiplier design.
- ❑ This TCL script will be launched using the Synopsys Design Compiler tool to synthesize your multiplier using the digital standard cells in the TSMC 65nm library.
- ❑ Run the Design Compiler GUI with the following Linux command: `design_vision`

2

- ❑ Perform the synthesis of your Verilog multiplier design by executing the synthesis script in Design Vision: File > Execute Script
- ❑ The compilation (compile_ultra) will take a few minutes to complete.
- ❑ Once complete, you will be able to view the gate-level schematic of your synthesized multiplier by right-clicking on the multiplier design in the Logical Hierarchy window and selecting schematic view.
- ❑ Save a copy of the schematic:
 - File > Print > Print to File (PDF).

3


- ❑ The Synopsys Design Compiler tool will output the following files into the working directory:
 - Synthesized Verilog netlist: multiplier_syn.v
 - Area constraint file: multiplier_syn.sdc
 - Timing and Area reports
- ❑ In your report, provide the generated estimates for total area and critical path timing.
- ❑ If you were to clock the design, what would be the maximum clock frequency?
- ❑ In your report, include the schematic of the synthesized multiplier, and highlight the critical path based on the timing report.

4

- ❑ Verify that your synthesis was successful by running the multiplier test bench with the newly-synthesized netlist and the TSMC 65nm standard cell Verilog technology file:
ncverilog testbench.v multiplier_syn.v tcbn65gplus.v
- ❑ Prior to running NCVerilog, ensure that all the module names in the generated Verilog files match.
- ❑ Provide the output of the NCVerilog test bench dialogue in your report.

Physical Implementation

 Get Ahead of the Curve with Innovus Implementation System




1

- ❑ Place the `innovus.globals` and `multiplier.view` file in the same working directory as the `multiplier_syn.v` and `multiplier_syn.sdc` files. Run the Cadence INNOVUS place & route tool with the following command: `innovus`
- ❑ Set up the design: File > Import Design > Load > `innovus.globals`
- ❑ This will load the appropriate timing and physical cell libraries for the place & route.


1

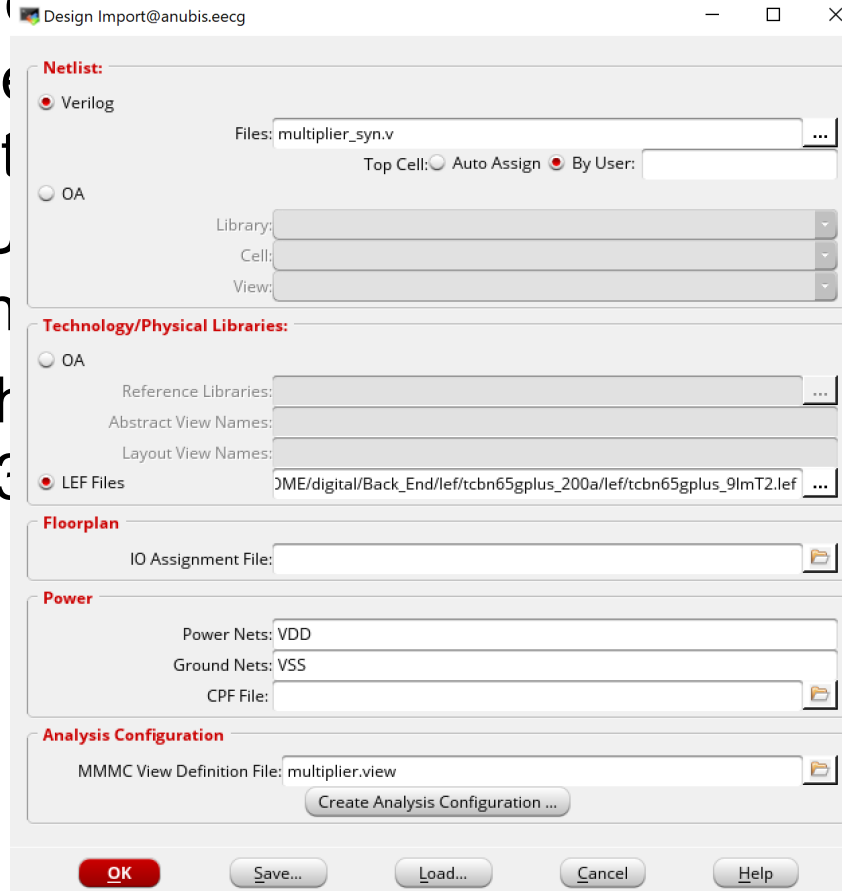- ❑ Place the innovus_global and multiplier.view file in the same directory as multiplier_syn.v and multiplier_syn.edi. Run the INNOVUS command line tool.
- ❑ Set up the multiplier_syn.v file in the innovus command line tool.
- ❑ This will load the multiplier_syn.v file and physical cell libraries.



2

 - ❑ Define Floorplan
- ❑ Use Edit > Pin Editor
 - Place A[] on left
 - Place B[] on right
 - Place product[] on top




2

❑ Place power stripes for VDD and VSS:

- Power > Power Planning
> Add Stripe
- Select the M3 Layer with:
Width: 1 and Spacing: 1
Select the M4 Layer with:
Width:1 and Spacing: 1
- Press Apply and OK.
- Set-to-set distance = 4

 ❑ You have now set up the power connections for the VDD and VSS rails.



Place and V

– Pow

> A

– Sel

Wic

Sel

Wic

– Pre

You h

power

VDD a

Add Stripes@anubis.eecg

Basic Advanced Via Generation Mode Preview

Set Configuration

Net(s): VDD VSS

Layer: M3(3) Directions: ☐ Vertical ☒ Horizontal

Width: 1 Spacing: 1

Set Pattern

☒ Set-to-set distance: 4 ☐ Number of sets: 1 ☐ Bumps

☐ Over P/G pins Pin layer: Top pin layer ▾ ☐ Pin Width:

☐ Master name: ☐ Selected blocks ☒ All blocks

☐ Over Physical Pins Pin layer: Top pin layer ▾ ☐ Pin Width:

Stripe Boundary

☒ Core ring ☐ Pad ring: Outer ▾ ☐ All domains

☐ Design boundary ☒ Create pins ☐ Each selected block/domain/fence

☐ Specify rectangular area

X1: Y1: X2: Y2:


☐ Specify rectilinear area

First/Last Stripe

Start from: ☐ Left ☐ Right ☐ Top ☒ Bottom


☒ Relative from core or selected area Start: Stop:

☐ Absolute Start: Stop:

 


3

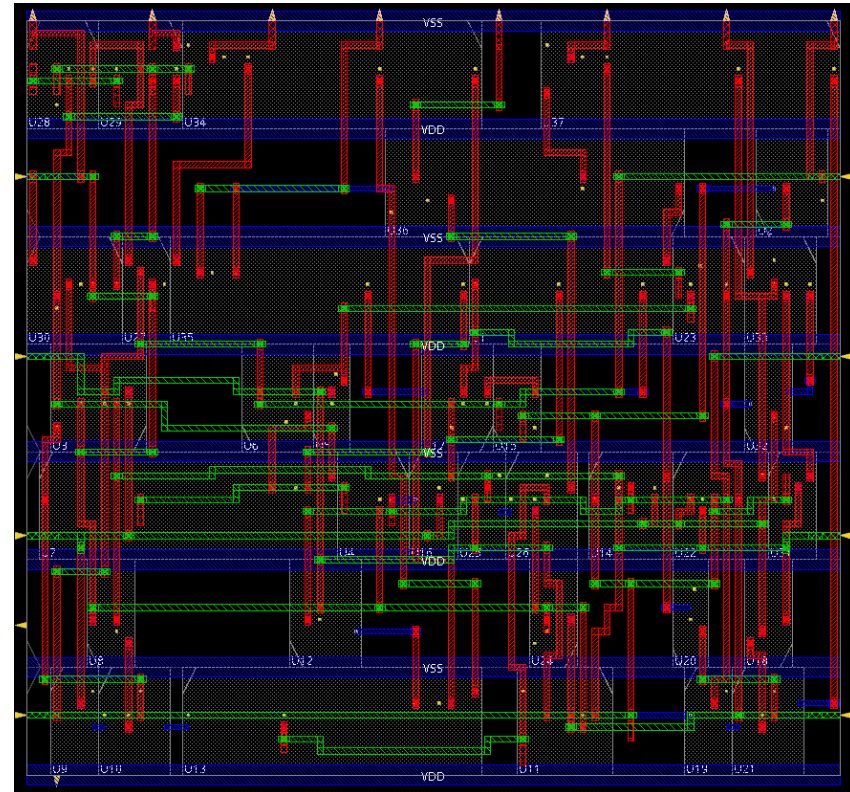- ❑ Place the standard cells:
 - Place > Place Standard Cell > OK
- ❑ Once complete, you can view the placed cells:
 - Place > Display > Display Spare Cell
- ❑ Verify that the design does not have any geometry errors:
 - Verify > Verify Geometry > OK



4

 - ❑ Route the power connections:
 - Route > Special Route
- ❑ You should now see VDD and VSS rails of standard cells connected to the VDD and VSS stripes
- ❑ Route the signal connections:
 - Route > NanoRoute
- ❑ Verify > Verify Geometry



- ☐ Route
- conn
- Ro
- ☐ You s
- VDD
- stand
- the V
- ☐ Route
- Ro
- ☐ Verify

Basic Advanced **Via Generation**

Net(s): VDD VSS ...

SRoute

☒ Block Pins ☒ Pad Rings ☒ Floating Stripes

☒ Pad Pins ☒ Follow Pins ☐ Secondary Power Pins

Routing Control

Layer Change Control

Top Layer: AP(10) ▶ Bottom Layer: M1(1) ▶

☒ Allow Jogging ☒ Allow Layer Change

☐ Specify Area

X1: Y1:

X2: Y2:

☐ Connect to Target Inside The Area Only

Power Domain Selection


☒ All ☐ Selected

☐ Named:

☐ Delete Existing Routes ☐ Generate Progress Messages

Mode Setup Target Editing Options




OK Apply Defaults Cancel Help

 

5

- ❑ Add filler cells to fill the unused area of your design:
 - Place > Physical Cell > Add Filler
 - Under Cell Name(s), select all the available filler cells from the cell list.
- ❑ Verify that the design does not have any geometry errors:
 - Verify > Verify Geometry > OK

- ❑ A cool feature to see congestion

   

6

- ❑ Perform a power analysis:
 - Power > Power Analysis > Run
- ❑ Perform static power analysis for a constant input activity factor of 0.2, over the frequency range of 100MHz to 1GHz.
- ❑ Plot your results for total internal power and total switching power vs. frequency on the same graph.
- ❑ Comment on these results with respect to the synthesized timing results obtained in Part 2.2.
- ❑ What do the power analysis estimates suggest is the maximum clock frequency?


7

- ❑ Obtain the total area of your placed & routed design:
File > Report > Summary
Compare the resulting total core area after place & route with the estimated synthesis area from Part 2.2. Comment on the discrepancy.

8

- ❑ Export the Verilog netlist of the placed & route design: File > Save > Netlist
- ❑ Save the file as multiplier_netlist.v, and verify that your synthesis was successful by running the multiplier test bench with the newly-synthesized netlist and the TSMC 65nm standard cell Verilog technology file:
ncverilog testbench.v multiplier_netlist.v
tcbn65gplus.v
- ❑ Provide the output of the NCVerilog test bench dialogue in your report.

Some Tips

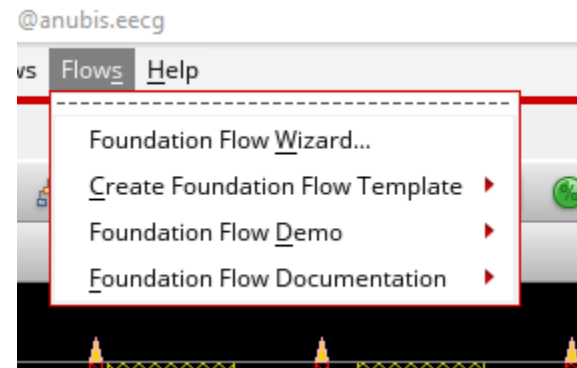

END