

ECE1388 VLSI Design Methodology

Lecture 10: Combinational Circuit Design


Outline

- ☐ Bubble Pushing
- ☐ Compound Gates
- ☐ Logical Effort Example
- ☐ Input Ordering
- ☐ Asymmetric Gates
- ☐ Skewed Gates
- ☐ Best P/N ratio

Example 1


```
module mux(input s, d0, d1,  
           output y);  
  
    assign y = s ? d1 : d0;  
endmodule
```

- 1) Sketch a design using AND, OR, and NOT gates.
Assume $\sim S$ is available.

 






Example 2

 2) Sketch a design using NAND, NOR, and NOT gates.
Assume $\sim S$ is available.




Bubble Pushing

- ❑ Start with network of AND / OR gates
- ❑ Convert to NAND / NOR + inverters
- ❑ Push bubbles around to simplify logic
 - Remember DeMorgan's Law

     

Example 3

 3) Sketch a design using one compound gate and one NOT gate. Assume $\sim S$ is available.





Compound Gates

□ Logical Effort of compound gates

unit inverter

$$Y = \overline{A}$$

 
 


$$g_A = 3/3$$

$$p = 3/3$$

AOI21

$$Y = \overline{A \cdot B + C}$$

  

$$g_A = 6/3$$



$$g_B = 6/3$$

$$g_C = 5/3$$

$$p = 7/3$$

AOI22

$$Y = \overline{A \cdot B + C \cdot D}$$

  

$$g_A = 6/3$$

$$g_B = 6/3$$



$$g_C = 6/3$$

$$g_D = 6/3$$

$$p = 12/3$$

Complex AOI
  
$$Y = \overline{A \cdot (B + C) + D \cdot E}$$



$$g_A = 5/3$$

$$g_B = 8/3$$

$$g_C = 8/3$$

$$g_D = 8/3$$


$$g_E = 8/3$$

$$p = 16/3$$

 Example 4

- ❑ The multiplexer has a maximum input capacitance of 16 units on each input. It must drive a load of 160 units. Estimate the delay of the two designs.

$$H = 160 / 16 = 10 \quad B = 1 \quad N = 2$$




$$P = 2 + 2 = 4$$

$$G = (4/3) \cdot (4/3) = 16/9$$

$$F = GBH = (16/9) \cdot 1 \cdot 10 = 17.8$$

$$\hat{f} = \sqrt[N]{F} = 4.2$$

$$D = N\hat{f} + P = 12.4\tau$$

 

$$P = 4 + 1 = 5$$

$$G = (6/3) \cdot (1) = 2$$

$$F = GBH = 20$$


$$\hat{f} = \sqrt[N]{F} = 4.5$$

$$D = N\hat{f} + P = 14\tau$$

 Example 5

- Annotate your designs with transistor sizes that achieve this delay.

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}} \Rightarrow C_{in_i} = \frac{C_{out_i} g_i}{\hat{f}}$$



$$C_{in1} = 16$$

$$C_{in2} = 160 * (4/3) / 4.2 = 50$$


Repeated from the previous slide:

$$g = 4/3$$

$$G = (4/3) \cdot (4/3) = 16/9; B = 1; H = 160/16 = 10$$

$$F = GBH = (16/9) \cdot 1 \cdot 10 = 17.8$$

$$\hat{f} = \sqrt[4]{F} = 4.2$$

 

$$C_{in1} = 16$$

$$C_{in2} = 60 * 1 / 4.5 = 36$$

(10.66 rounded to 10, 5.33 rounded to 6; Sum=16)



$$g = 1$$

$$G = (6/3) \cdot (1) = 2; B = 1; H = 160/16 = 10$$

$$F = GBH = 20$$

$$\hat{f} = \sqrt[4]{F} = 4.5$$

Recall: Input Order

 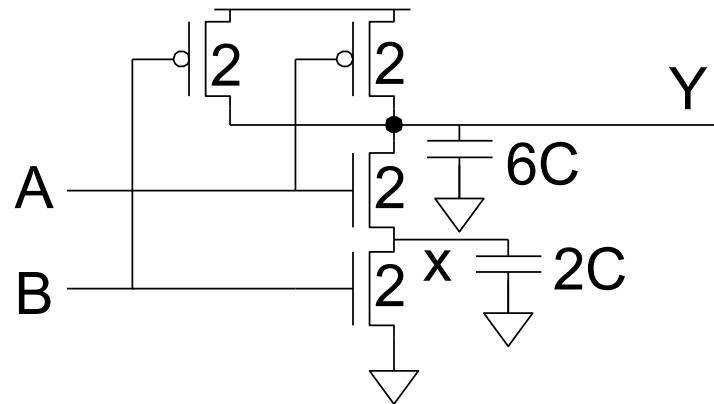

❑ Calculate *parasitic delay* for Y falling

- If A arrives latest? 2τ (node x already discharged)

$$t_{pdf} = \left[(6 + 4h)C \right] \left(\frac{R}{2} + \frac{R}{2} \right) = (6 + 4h)RC$$


- If B arrives latest? 2.33τ (node x not discharged)

$$t_{pdf} = (2C) \left(\frac{R}{2} \right) + \left[(6 + 4h)C \right] \left(\frac{R}{2} + \frac{R}{2} \right) = (7 + 4h)RC$$

$$d = t_{pdf} / 3RC \text{ and } h = 0$$



Inner & Outer Inputs

 - ❑ *Inner* input is closest to output (A)
- ❑ *Outer* input is closest to rail (B)
- ❑ If input arrival time is known
 - Connect latest input to inner terminal




Asymmetric Gates

- ❑ Asymmetric gates **favor one input over another**
- ❑ Ex: suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same
- ❑ $g_A = (2+4/3)/3=10/9$ (**$< 4/3=12/9$ for symmetric NAND2**)
- ❑ $g_B = 6/3=2$ (for reset input)
- ❑ $g_{\text{total}} = g_A + g_B = 28/9$
 (**$> 4/3+4/3=24/9$**)
- ❑ Asymmetric gate can approach $g = 1$ on critical input
- ❑ But total logical effort goes up

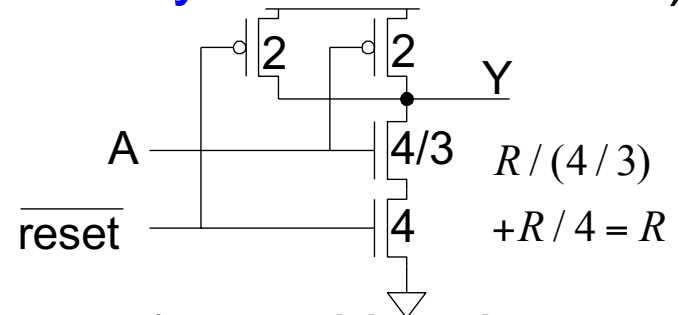 


Symmetric Gates

- Inputs can be made perfectly symmetric

 

Skewed Gates

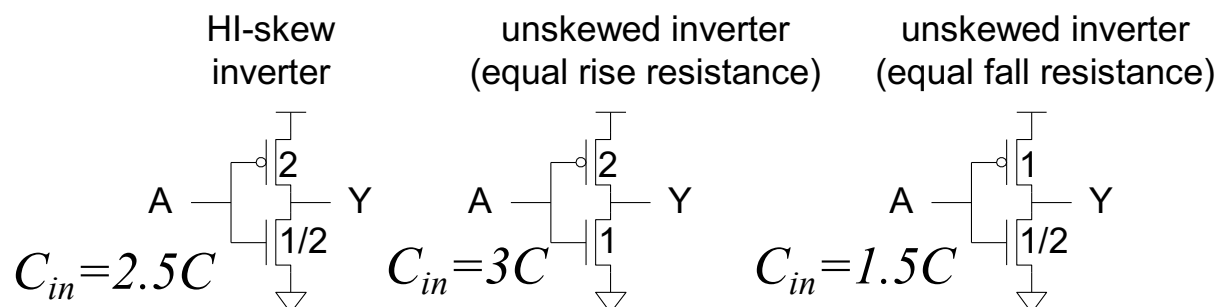- ❑ Skewed gates favor one edge over another
- ❑ Ex: suppose the rising output of inverter is most critical
 - Downsize noncritical nMOS transistor



- ❑ Calculate logical effort by comparing to *unskewed* inverter with same effective resistance on that edge.
 - $g_u = 2.5 / 3 = 5/6 < 1 \rightarrow$ improved vs unit inverter
 - $g_d = 2.5 / 1.5 = 5/3 > 1 \rightarrow$ worse vs unit inverter
 - $g_{ave} = (5/6 + 5/3)/2 = 5/4 > 1 \rightarrow$ worse vs unit inverter


HI- and LO-Skew

- ❑ Def: Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition.
- ❑ Skewed gates reduce size of noncritical transistors
 - HI-skew gates favor rising output (small nMOS)
 - LO-skew gates favor falling output (small pMOS)
- ❑ Logical effort is smaller for favored direction
- ❑ But larger for the other direction


Catalog of Skewed Gates

Inverter


unskewed

 




HI-skew

 




LO-skew

 

NAND2

  
 


NOR2

   


Asymmetric Skew

  - ❑ Combine asymmetric and skewed gates
 - Downsize noncritical transistor on unimportant input
 - Reduces parasitic delay for critical input



Best P/N Ratio for Min Delay

- ❑ For best noise margins we have selected $W_p/W_n = \mu_n/\mu_p$
 - e.g., $\mu_n/\mu_p = 2$ in textbook
- ❑ For least average delay, choose $W_p/W_n = \sqrt{\mu_n/\mu_p}$
- ❑ Proof for inverter with no load
 - Define $\mu = \mu_n/\mu_p$; P is size parameter (not paras. delay)
 - $t_{pdf} = RC_{out} = P+1$ - as $C_{out} = P+1$ and $R=1$ for NMOS
 - $t_{pdr} = (P+1)(\mu/P)$ - as xP wider but $x\mu$ slower
 - $t_{pd} = (P+1)(1+\mu/P)/2 = (P + 1 + \mu + \mu/P)/2$
 - $dt_{pd} / dP = (1 - \mu/P^2)/2 = 0$
 - Least delay for $P = \sqrt{\mu} = \sqrt{\mu_n/\mu_p}$

 


Preferred P/N Ratios


- ❑ Often, best P/N ratio is chosen as $W_p/W_n = \sqrt{\mu_n/\mu_p}$
 - Degrades noise margin somewhat
 - Only improves average delay *slightly* for inverter
 - But **significantly decreases area and power**
- ❑ Ex: **inverter** - **best speed**, good area/power/noise-tolerance
NAND: **best noise-tolerance**, good speed/area/power
NOR: **good area/speed/power**; lower noise-tolerance

Inverter


fastest
P/N ratio

 

NAND2

 

NOR2

 

Observations

- ❑ For speed:
 - NAND vs. NOR
 - Many simple stages vs. fewer high fan-in stages
 - Delay-critical input
 - Should be connected closest to the output
- ❑ For area and power:
 - Many simple stages vs. fewer high fan-in stages