

ECE1388 VLSI Design Methodology

Lecture 5: DC & Transient Response

Outline

- ☐ DC Response
- ☐ Logic Levels and Noise Margins
- ☐ Transient Response
- ☐ Delay Estimation

DC Response

□ DC Response: V_{out} vs. V_{in} for a gate

□ Ex: Inverter

– When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$

– When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$


– In between, V_{out} depends on transistor size and current

– By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

– We could solve equations

 – But graphical solution gives more insight



Transistor Operation


- ❑ Current depends on region of transistor behavior
- ❑ For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


I-V Characteristics

 - Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

 


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in

 


Load Line Analysis

□ $V_{in} = 0$

 


Load Line Analysis

□ $V_{in} = 0.2V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.4V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.6V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.8V_{DD}$

 


Load Line Analysis

□ $V_{in} = V_{DD}$



 


Load Line Summary

 

DC Transfer Curve

  
 
- Transcribe points onto V_{in} vs. V_{out} plot



Operating Regions

□ Revisit transistor operating regions



Region	nMOS	pMOS
A		
B		
C		
D		
E		

  

Operating Regions


□ Revisit transistor operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

  


Beta Ratio

 - ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed gate*
- ❑ Other gates: collapse into equivalent inverter




Noise Margins

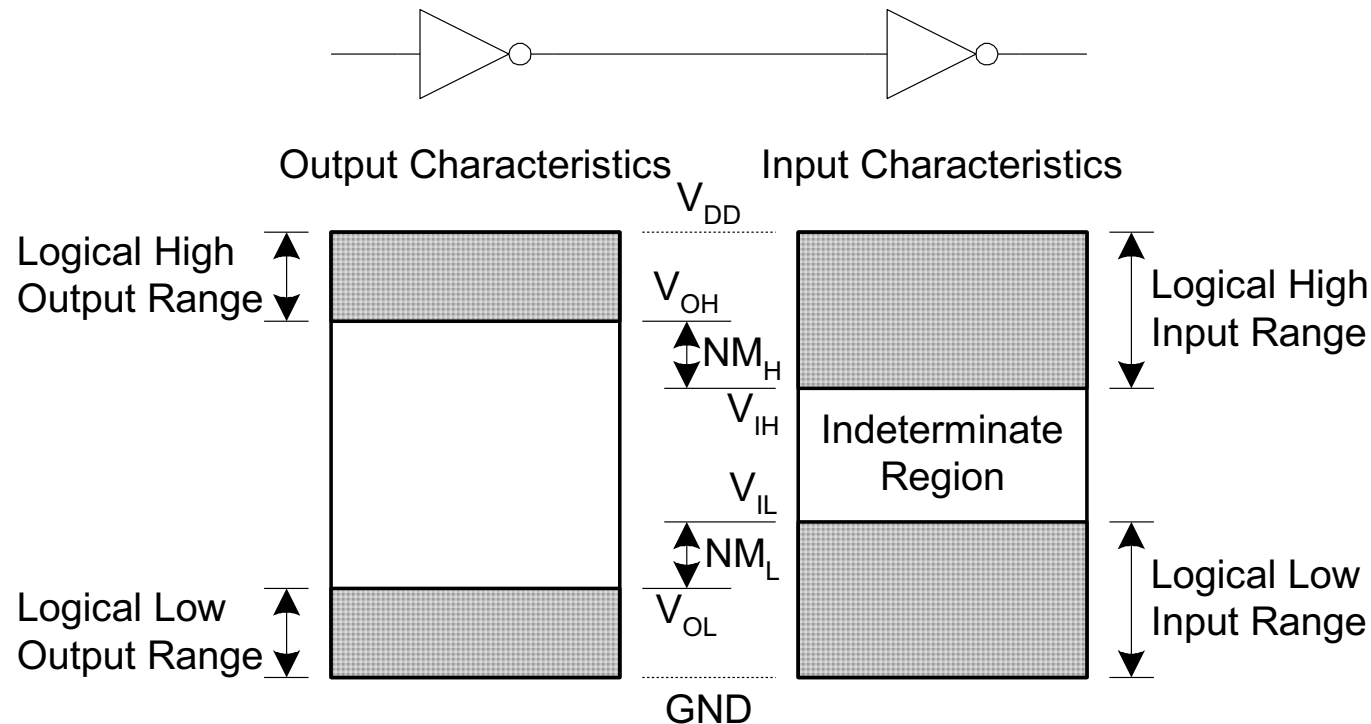- ❑ How much noise can a gate input see before it does not recognize the input?




Logic Levels

 - ❑ To maximize noise margins, select logic levels at



Logic Levels

 - ❑ To maximize noise margins, select logic levels at
 - unity gain point of DC transfer characteristic



For best noise margins:

$$W_p/W_n = \mu_n/\mu_p$$

For highest density:

$$W_p/W_n = 1 - \text{min size}$$

Btw, for highest speed:

$$W_p/W_n = (\mu_n/\mu_p)^{1/2}$$

(The last formulae is a preview of what's to come: it will be derived in lecture 10, slide 18;

An alternative proof is also available in K. Martin, Digital Integrated Circuits Design, p. 208)

Transient Response

- ❑ *DC analysis* tells us V_{out} if V_{in} is constant
- ❑ *Transient analysis* tells us $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations
- ❑ Input is usually considered to be a step or ramp
 - From 0 to V_{DD} or vice versa

Inverter Step Response



□ Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
 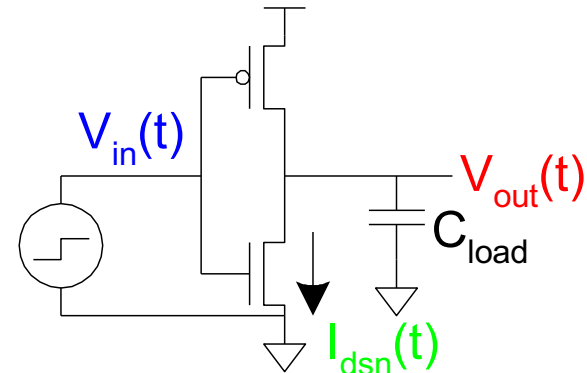
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Definitions

Propagation delay: maximum time

- ❑ t_{pdr} : *rising propagation delay*
 - From input to rising output, both crossing $V_{DD}/2$
- ❑ t_{pdf} : *falling propagation delay*
 - From input to falling output, both crossing $V_{DD}/2$
- ❑ t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- ❑ t_r : *rise time*
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- ❑ t_f : *fall time*
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$


Delay Definitions

Contamination delay: minimum time

- ❑ t_{cdr} : *rising contamination delay*
 - From input to rising output, both crossing $V_{DD}/2$
- ❑ t_{cdf} : *falling contamination delay*
 - From input to falling output, both crossing $V_{DD}/2$
- ❑ t_{cd} : *average contamination delay*
 - $t_{pd} = (t_{cdr} + t_{cdf})/2$

Simulated Inverter Delay

 - ❑ Solving differential equations by hand is too hard
- ❑ SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- ❑ But simulations take time to write up/set up





Delay Estimation

- ❑ We would like to be able to easily estimate delay
 - Not as accurate as simulation
- ❑ The step response usually looks like a 1st order RC response with an **asymptotically settling exponential**
- ❑ Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- ❑ Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC Delay Models

  - ❑ Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , cap C on each node
 - Unit pMOS has resistance $2R$, cap C on each node
- ❑ Capacitance - proportional to width
- ❑ Resistance - inversely proportional to width




Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).




3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




3-input NAND Caps

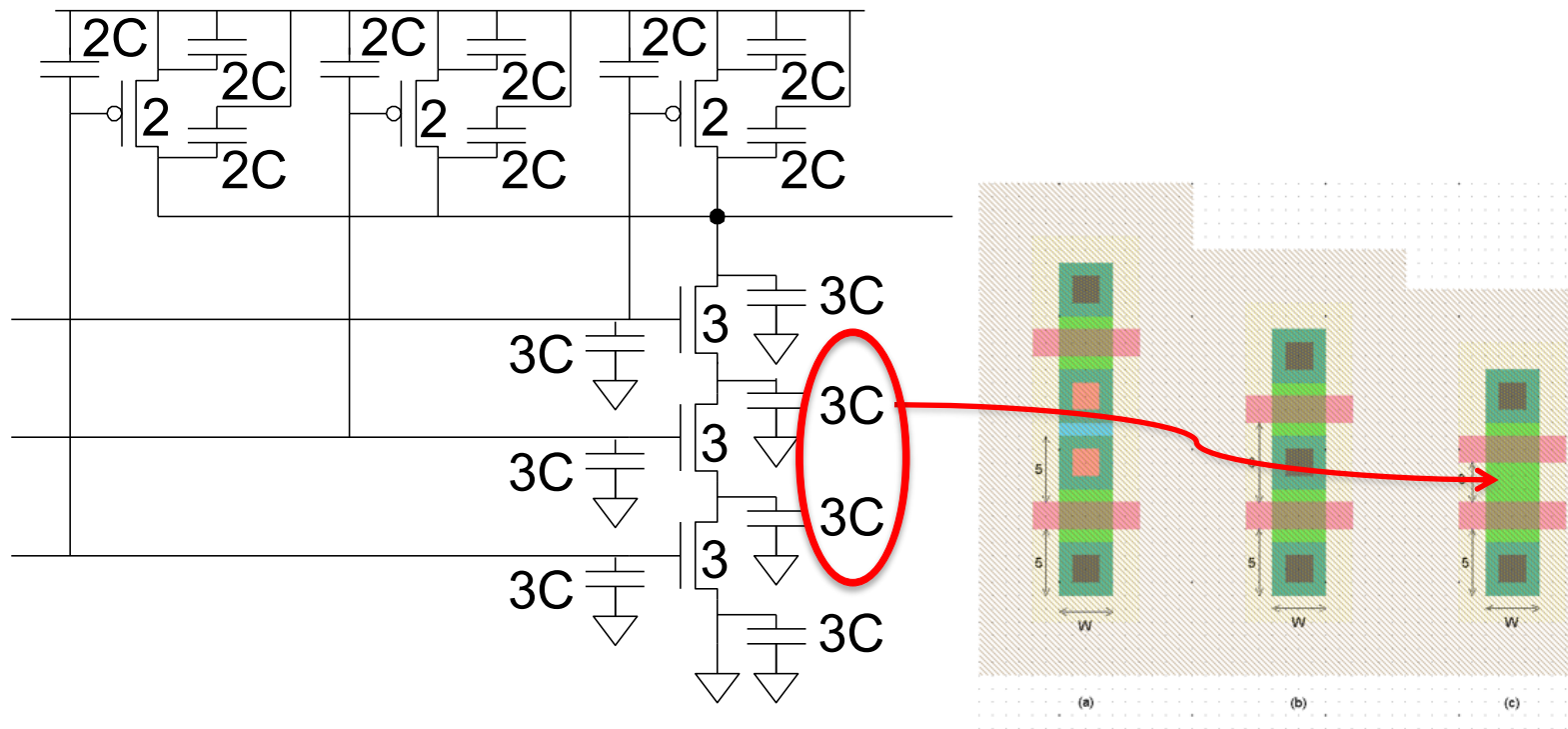- Annotate the 3-input NAND gate with gate and diffusion capacitance.



3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ❑ ON transistors look like resistors
- ❑ Pullup or pulldown network modeled as *RC ladder*
- ❑ Elmore delay of RC ladder

$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$

 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



- ❑ For branched networks only “in-signal-path” R counts


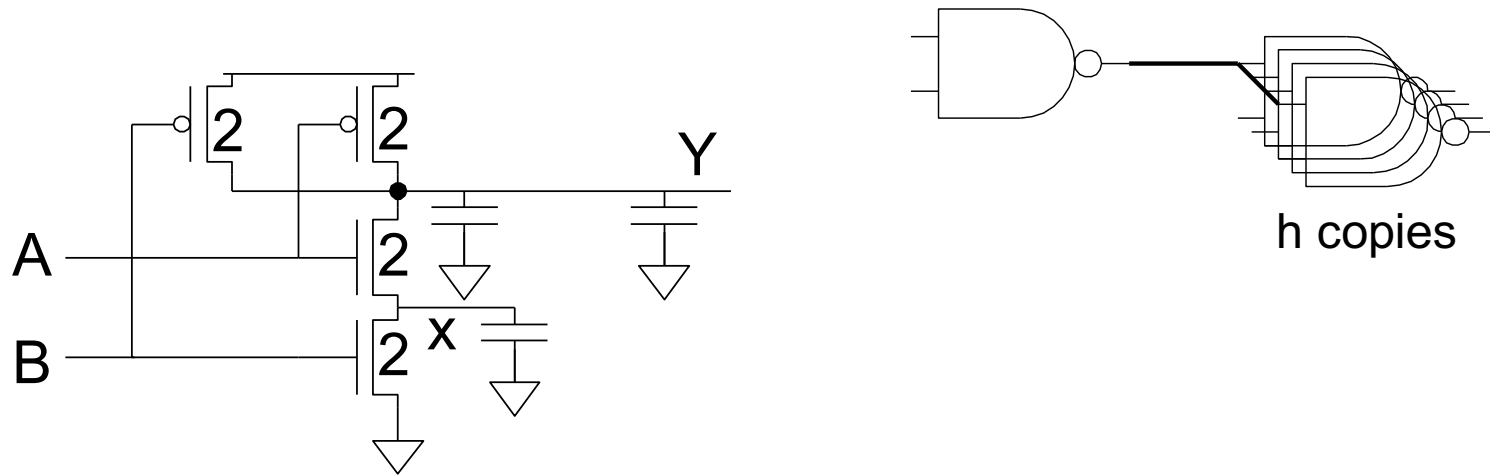
Example: 2-input NAND

- Estimate rising and falling worst-case (propagation) delays of a 2-input NAND driving h identical gates.



 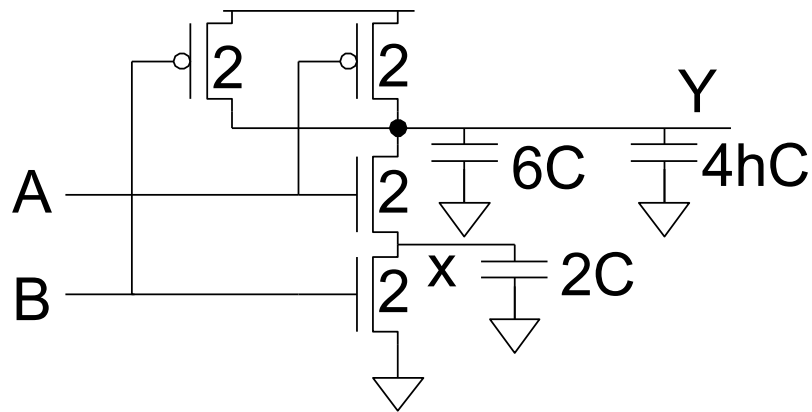
Example: 2-input NAND

- Estimate rising and falling worst-case (propagation) delays of a 2-input NAND driving h identical gates.



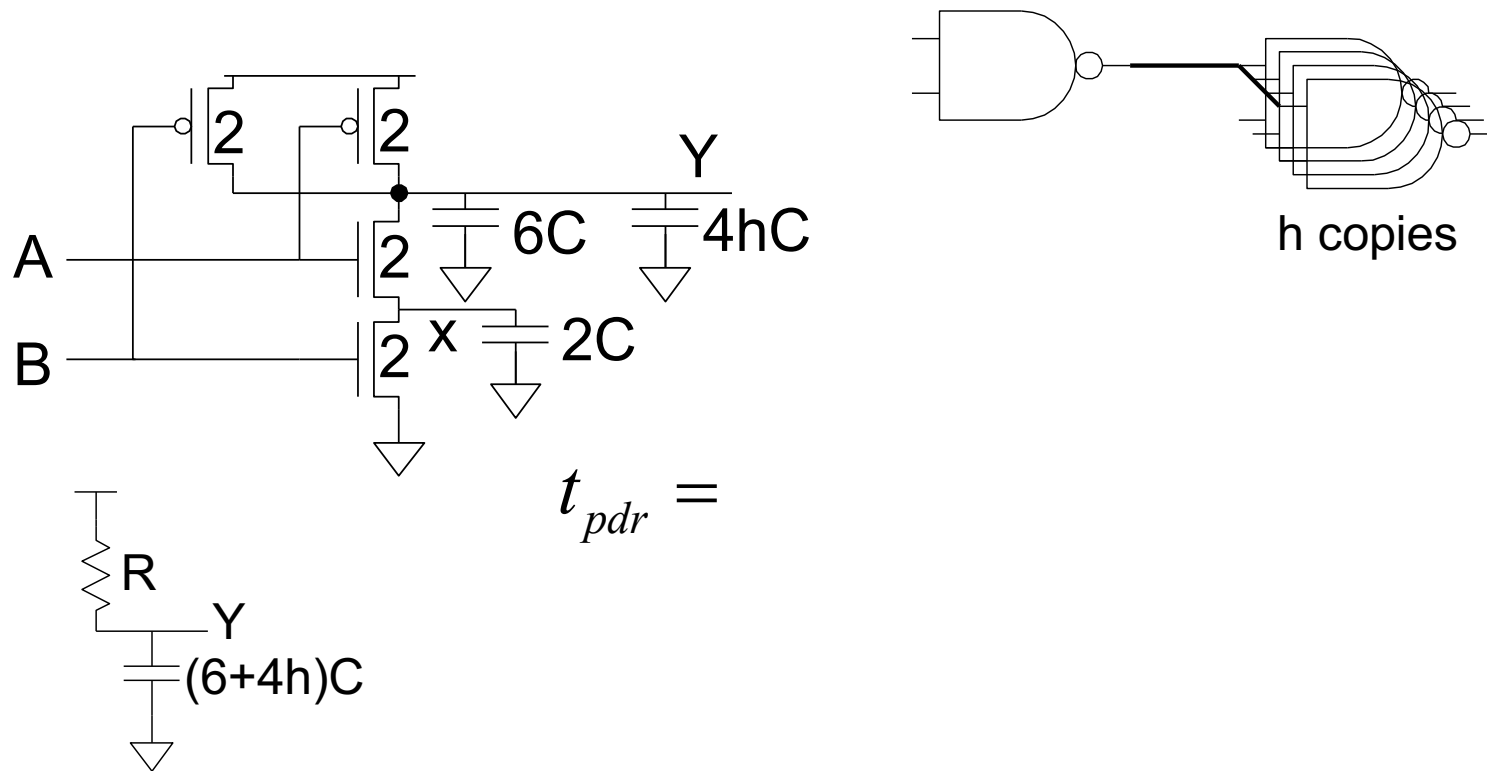
Example: 2-input NAND

- Estimate **rising** and falling worst-case (propagation) delays of a 2-input NAND driving h identical gates.




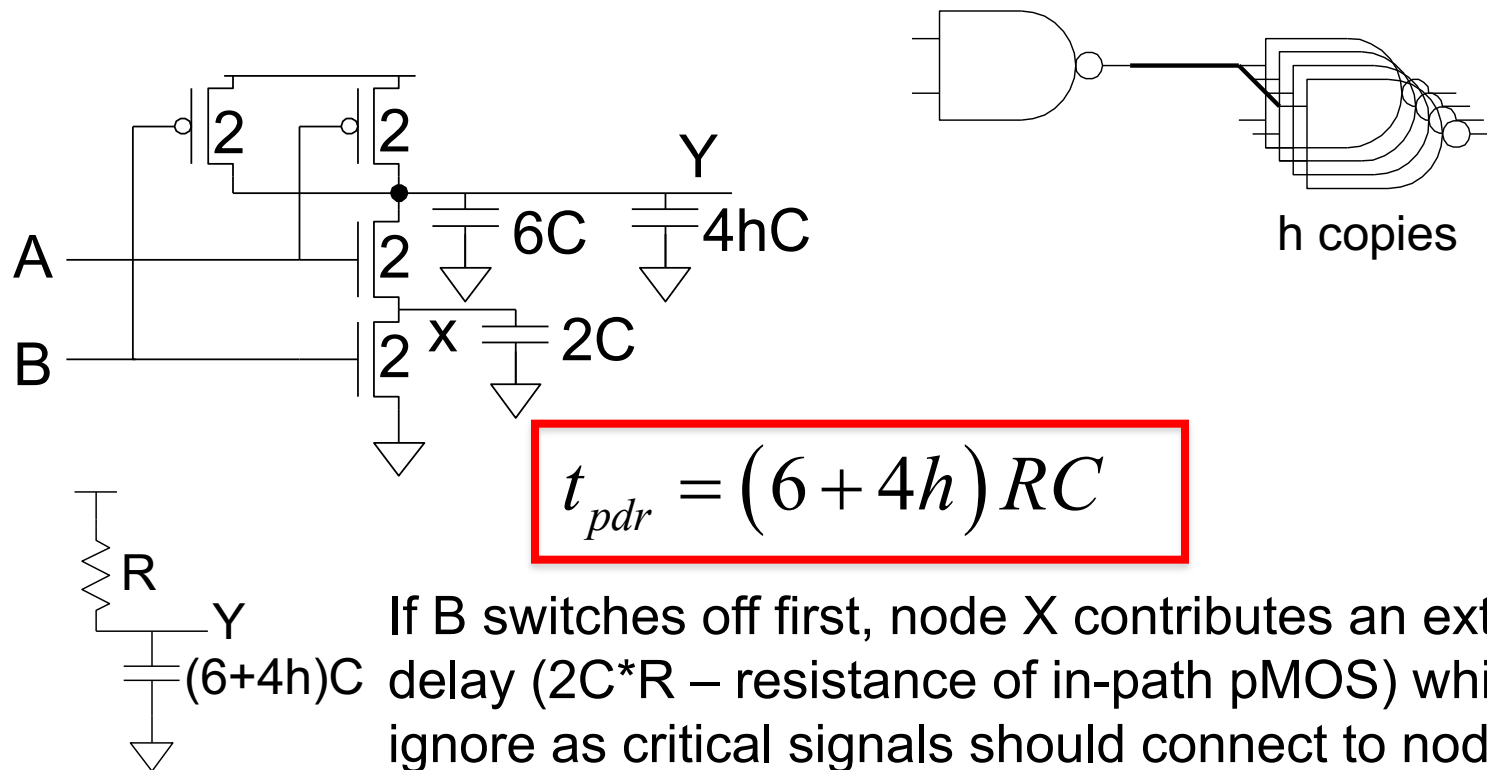
Example: 2-input NAND

- Estimate **rising** and falling worst-case (propagation) delays of a 2-input NAND driving h identical gates.




 
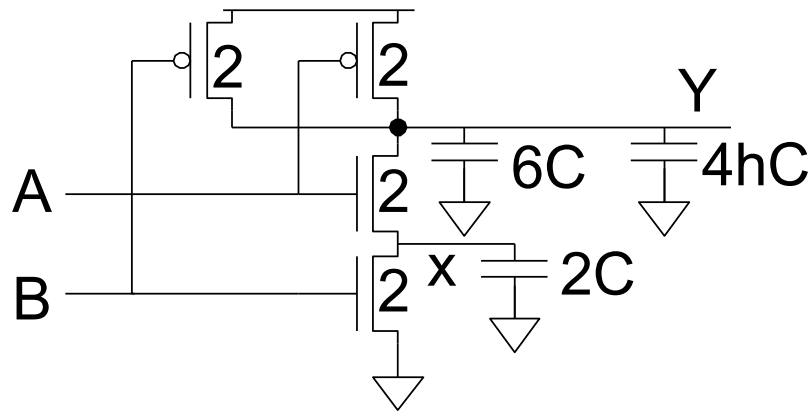
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



  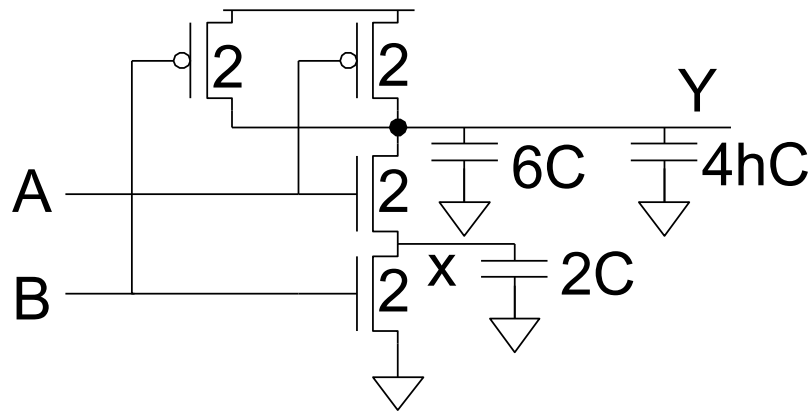Example: 2-input NAND



- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



$$t_{pdf} =$$


Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.
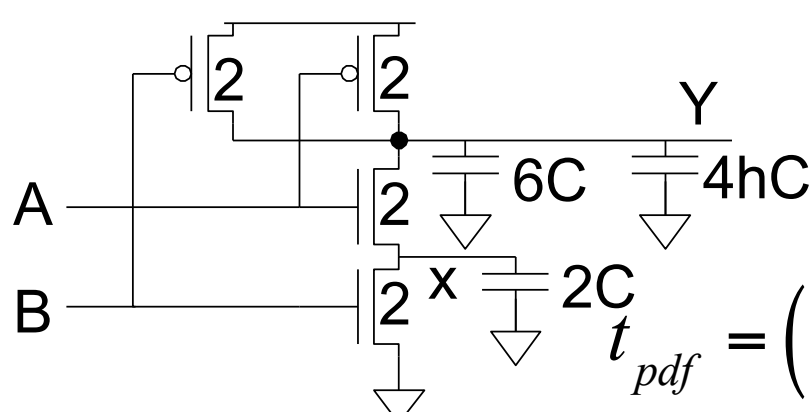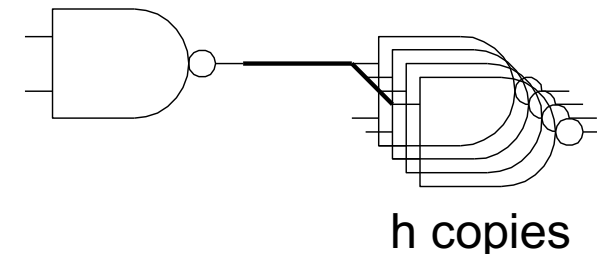
$$t_{pdf} = (2C)\left(\frac{R}{2}\right) + \left[(6 + 4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right)$$

$$= (7 + 4h)RC$$

 

If A arrives last, node X is already discharged and we ignore it:


$$t_{pdf} = (6 + 4h)RC$$

Delay Components

- ❑ Delay has two parts
 - *Parasitic delay*
 - $6RC$
 - Independent of load
 - *Effort delay*
 - $4hRC$
 - Proportional to load capacitance

Contamination Delay


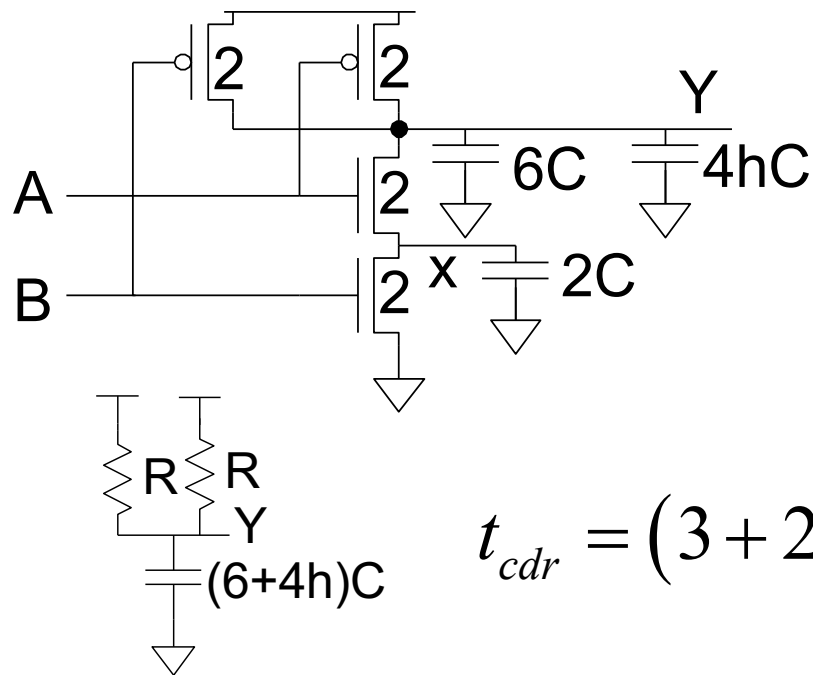
- ❑ Best-case (contamination) delay can be substantially less than propagation delay.
- ❑ Ex: If both inputs fall simultaneously



$$t_{cdr} = (3 + 2h)RC$$

Diffusion Capacitance

  - ❑ we assumed contacted diffusion on every s / d.
- ❑ Good layout minimizes diffusion area
- ❑ Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



($7C$, not $9C$ when assuming contacted s / d)

Layout Comparison

❑ Which layout is better?

