

ECE1388 VLSI Design Methodology


Lecture 6: Logical Effort

Outline

- ❑ Introduction
- ❑ Delay in a Logic Gate
- ❑ Multistage Logic Networks
- ❑ Choosing the Best Number of Stages
- ❑ Example
- ❑ Summary

Introduction

- ❑ Chip designers face a bewildering array of choices
 - *What is the **best circuit topology** for a function?*
 - *How many stages of logic give least delay?*
 - *How wide should the transistors be?*
- ❑ **Logical effort** is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries
 - A valuable academic method that helps develop intuition
 - In practice (ie. Industry) - used only for inverters, not other gates

 

Delay in a Logic Gate


- Express delays in **process-independent unit**

$$d = \frac{d_{abs}}{\tau}$$

$\tau = 3RC$ - unit inverter delay
without load

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

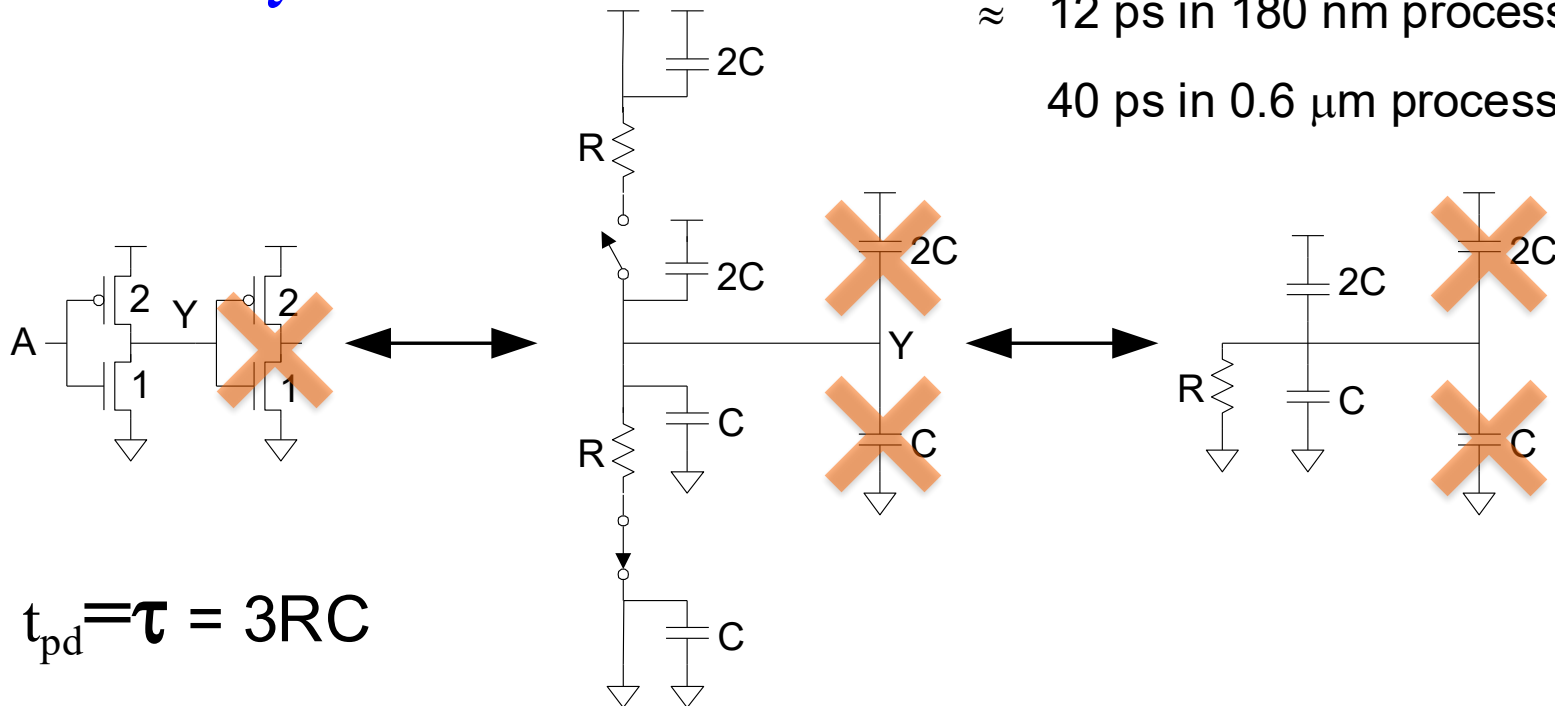

$$t_{pd} = \tau = 3RC$$

Delay in a Logic Gate

- Delay has two components

$$d = f + p$$

- **Effort delay** $f = gh$ (*a.k.a.* stage effort)

- g : **logical effort**

- Measures relative ability of gate to deliver current
- $g \equiv 1$ for inverter

- h : **electrical effort** $= C_{\text{out}} / C_{\text{in}}$

- Ratio of output to input capacitance (*a.k.a.* fanout)

Delay in a Logic Gate

- Delay has two components

$$d = f + p$$

- **Effort delay** $f = gh$ (*a.k.a.* stage effort)

- g : **logical effort**

- Measures *relative* ability of gate to deliver current
- $g \equiv 1$ for inverter

- h : **electrical effort** $= C_{\text{out}} / C_{\text{in}}$



- Ratio of output to input capacitance (*a.k.a.* fanout)

- **Parasitic delay** p


- Represents delay of gate driving no load
- Set by internal parasitic capacitance

Recall: 2-input NAND t_{pdr}

 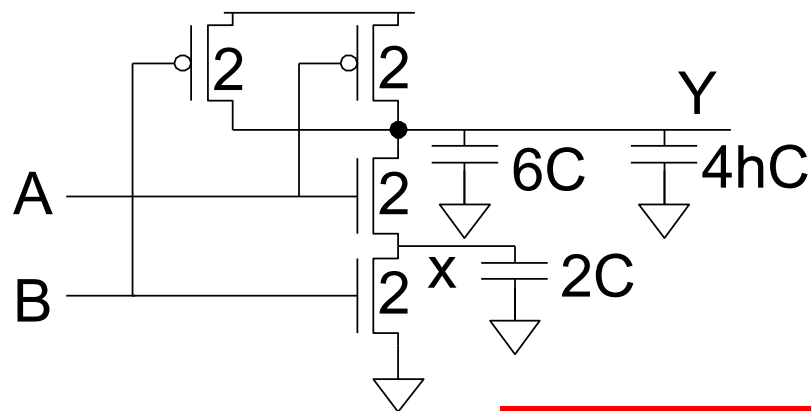- Estimate **rising** and falling worst-case (propagation) delays of a 2-input NAND driving h identical gates.





$$t_{pdr} = (4h + 6)RC$$

 

This is valid for signal A, ie A switches off first.
 For signal B, ie if B switches off first, node X contributes an extra $2RC$ delay ($2C \cdot R$ – resistance of in-path pMOS) which we ignore as critical signals should be connected to node A.


Recall: 2-input NAND t_{pdf}

 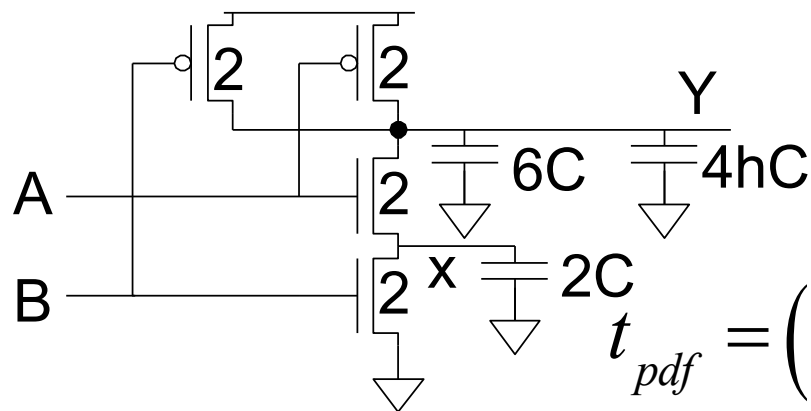- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



$$t_{pdf} = (2C)\left(\frac{R}{2}\right) + (6 + 4h)C\left(\frac{R}{2} + \frac{R}{2}\right)$$
 
$$= (7 + 4h)RC \quad \text{Valid if signal B turns on last.}$$




If A turns on last, node X is precharged and we ignore it:

$$t_{pdf} = (4h + 6)RC$$

$$d = ((t_{pdr} + t_{pdf}) / 2) / 3RC = 4 / 3h + 2$$

Delay Plots

$$d = f + p$$
$$= gh + p$$

 

Delay Plots

$$d = f + p$$

$$= gh + p$$


□ NAND2 (from past lecture & review):

$$d = (4h+6)RC / 3RC$$

$$= (4/3)h + 2$$


τ

□ What about NOR2?

 


Computing Logical Effort

 
- ❑ DEF: Logical effort is the *ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current*.
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Catalog of Gates

□ Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

Catalog of Gates


❑ Parasitic delay of common gates

– In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$


Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

The FO4 delay is about

200 ps in 0.6 μm process

60 ps in a 180 nm process

$f/3$ ns in an f μm process

Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort*

$$G = \prod g_i$$

Recall:

$$d = f + p$$

❑ *Path Electrical Effort*


$$H = \frac{C_{out-path}}{C_{in-path}}$$

$$= gh + p$$

❑ *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

 ❑ Can we write $F = GH$? **Only if there are no branches!**



Paths that Branch

□ Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 

Branching Effort

- ❑ Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- ❑ Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ❑ Path Effort Delay $D_F = \sum f_i$
- ❑ Path Parasitic Delay $P = \sum p_i$
- ❑ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N -stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- **Working backward**, apply capacitance transformation to find input capacitance of each gate given the load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort $G =$

Electrical Effort $H =$

Branching Effort $B =$


Path Effort $F =$

Best Stage Effort $\hat{f} =$

Parasitic Delay $P =$

Delay $D =$

Example: 3-stage path

 

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay

$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$


Example: 3-stage path

- Work backward for sizes, use $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$

y =

x =
 
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$




Example: 3-stage path

- Work backward for sizes, use $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$

$$y = (5/3) * 45 / 5 = 15$$

$$x = (5/3) * (15 * 2) / 5 = 10$$
 
$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$




Example: 3-stage path

- Work backward for sizes


$$y = (5/3) * 45 / 5 = 15$$

$$x = (5/3) * (15 * 2) / 5 = 10$$

 


$$C_{in} = 3$$
$$g = 3/3$$

$$W_p/W_n=1$$

 

$$C_{in} = 4$$
$$g = 4/3$$

$$W_p/W_n=4$$

 

$$C_{in} = 5$$
$$g = 5/3$$


Two equations and two unknowns – solve for W_p and W_n

Example: 3-stage path

- Work backward for sizes

$$y = (5/3) * 45 / 5 = 15$$


$$x = (5/3) * (15 * 2) / 5 = 10$$

 

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter ($F=64/1=64$)

D =

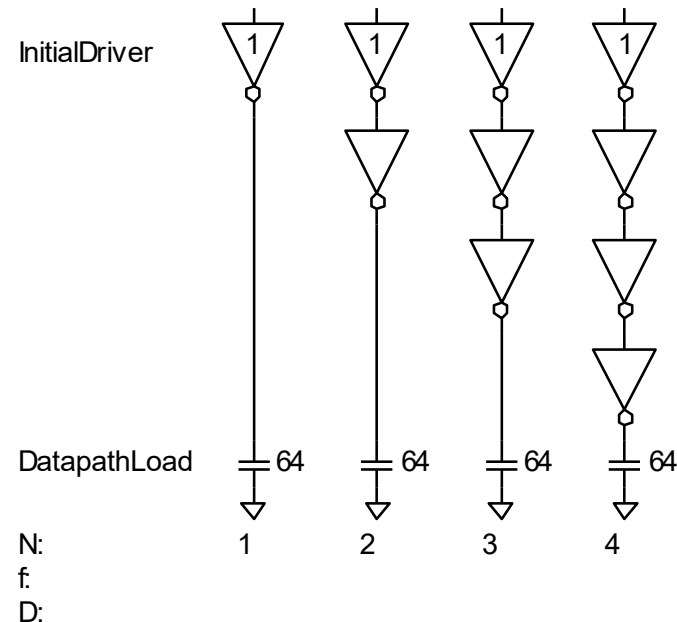


Best Number of Stages

- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter (F=64/1=64)

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

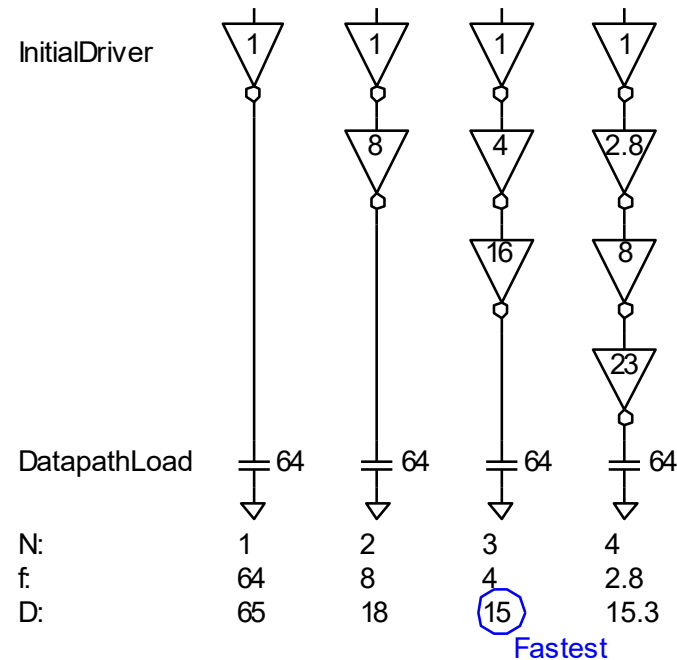

Derivation

- Consider adding inverters to end of path
 - How many give least delay?


$$D = NF^{\frac{1}{N}} + Np_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

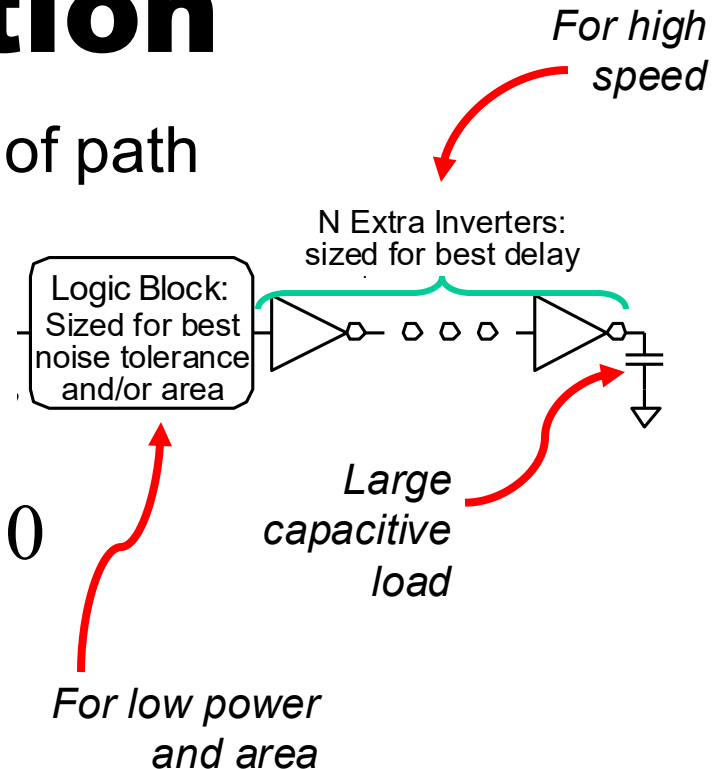- This is the approach preferred in practice (to save power):
 - Logic: sized for best noise tolerance, area (min-size NMOS)
 - Followed by inverter chain: sized for minimal delay




Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 - How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can round up from $\rho = 3.59$ to $\rho = 4$
 - accounts for wire parasitics etc.

Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- ❑ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ❑ Simplistic delay model
 - Neglects input rise time effects
- ❑ Interconnect
 - Iteration required in designs with wire
- ❑ Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- ❑ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters (and NAND2) best for driving large caps
- ❑ Provides language for discussing fast circuits
 - An academic method that helps develop intuition
 - In industry - used only for inverters, not other gates