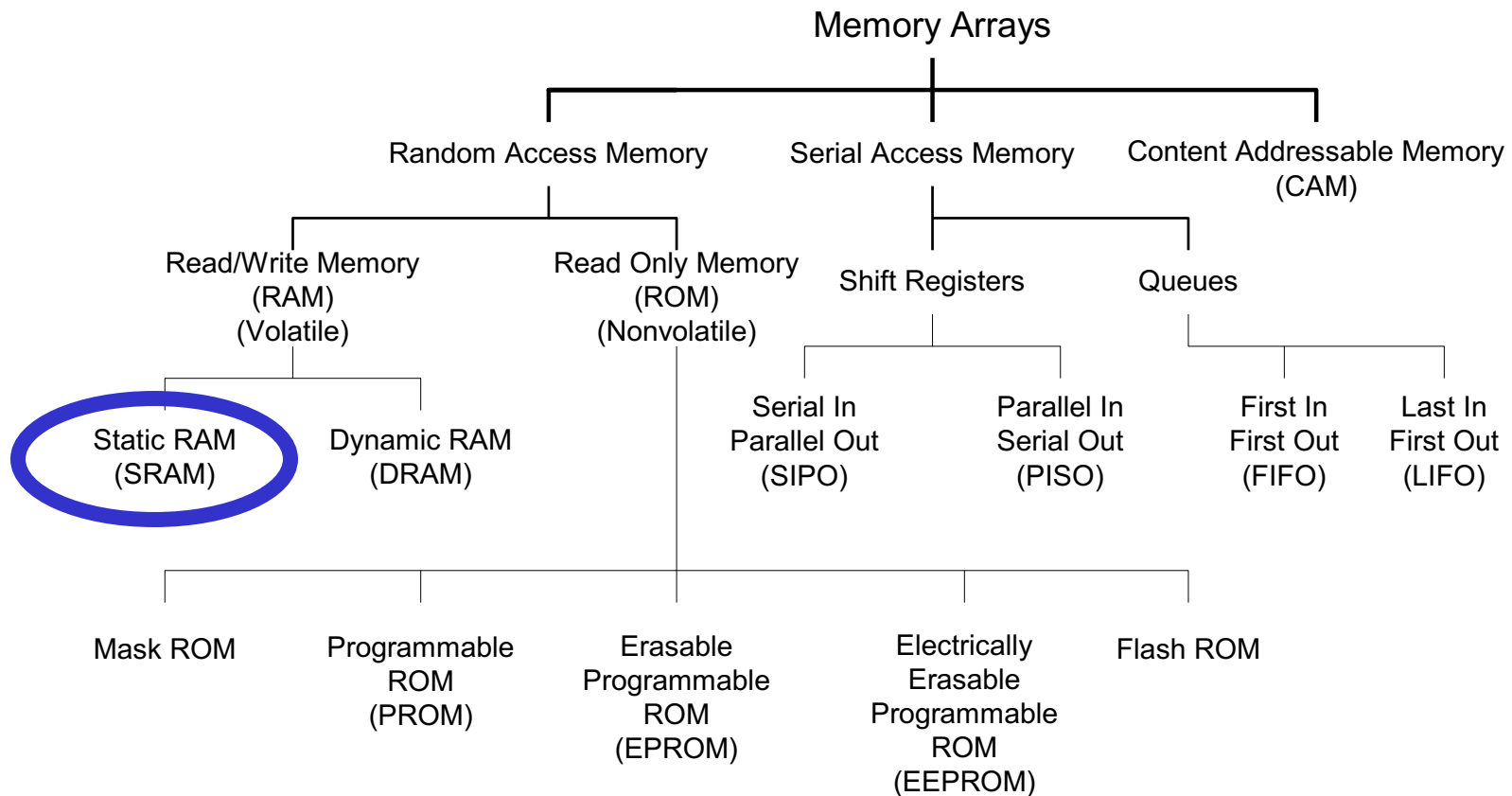


ECE1388 VLSI Design Methodology


Lecture 14

Memories II: DRAM, ROM, CAM



Memory Arrays




Memory Arrays

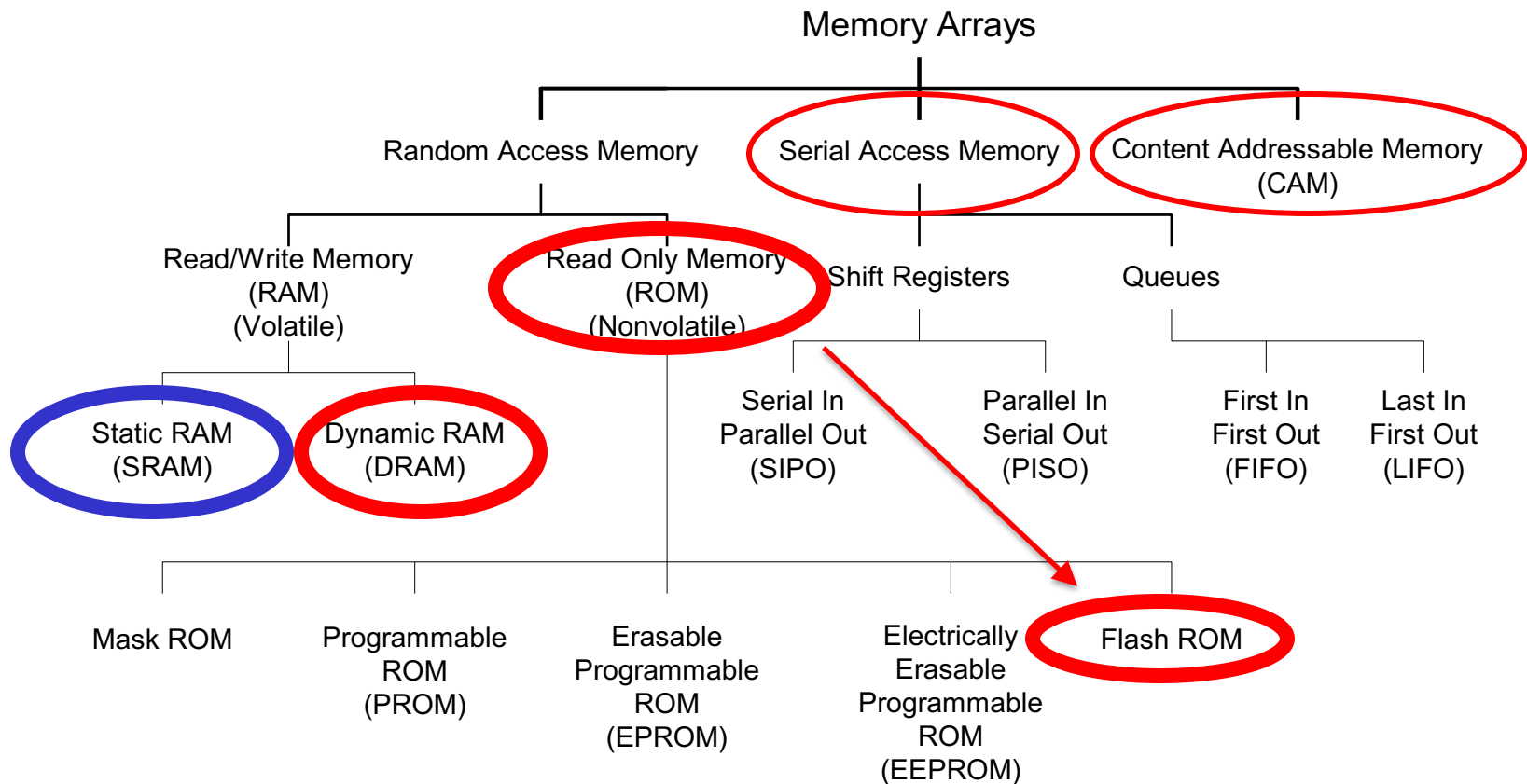

Semiconductor Memories

  



Wikipedia

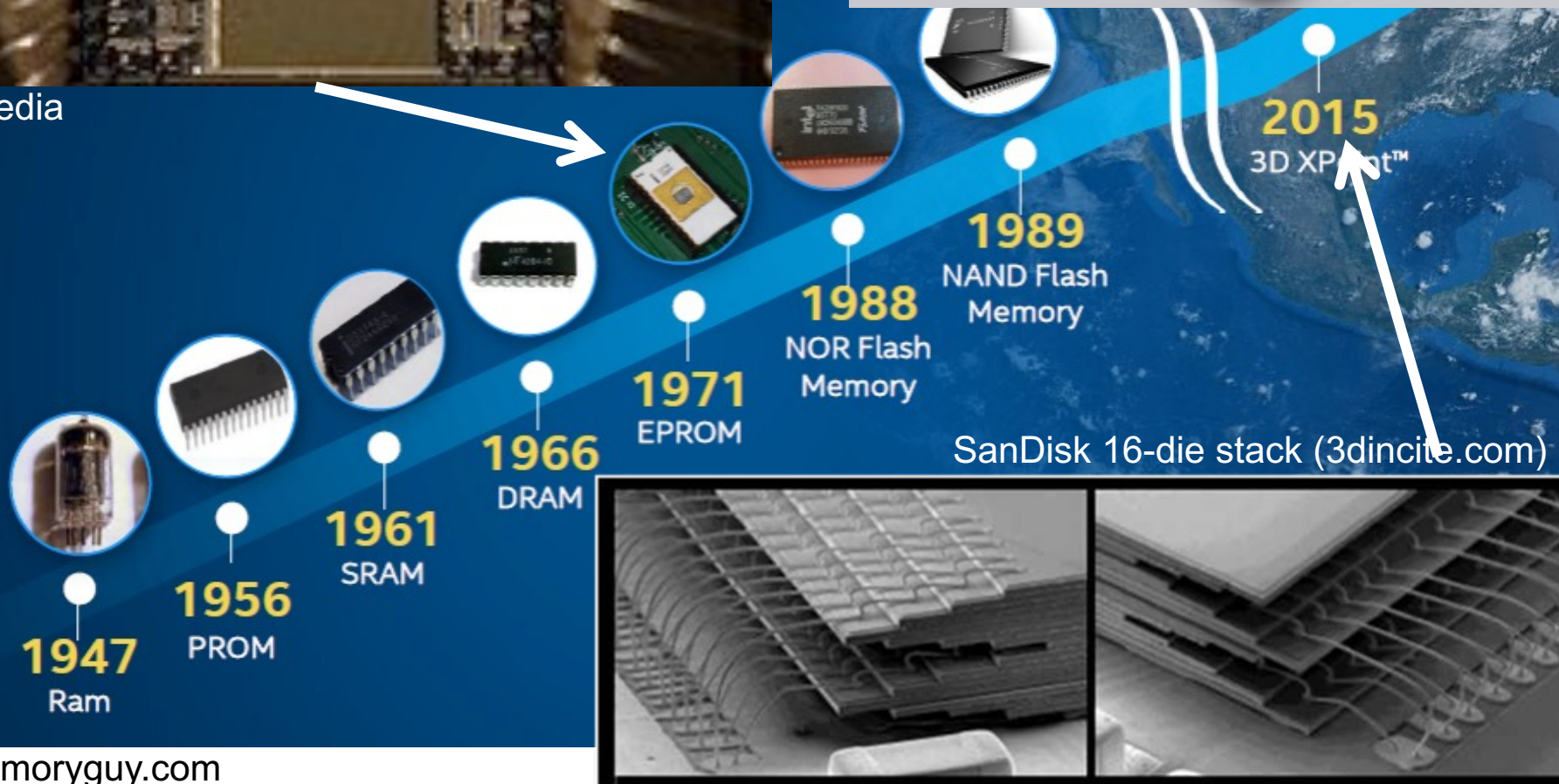

Outline

- ❑ DRAM
- ❑ Read-Only Memories (ROM), including Flash
- ❑ Serial Access Memories
- ❑ Content-Addressable Memories (CAM)

SRAM vs. DRAM

  


- ❑ SRAM: 6T per bit
 - built with standard **high-speed** CMOS technology

- ❑ DRAM: 1T per bit
 - built with special DRAM process optimized for **density**


Adapted from Prof. M. Prvulovic CS 4290/6290 notes are Georgia Tech

DRAM Capacitor

 

Adapted from Prof. Nikolic EECS141/2003 notes from UC-Berkeley


DRAM Bank

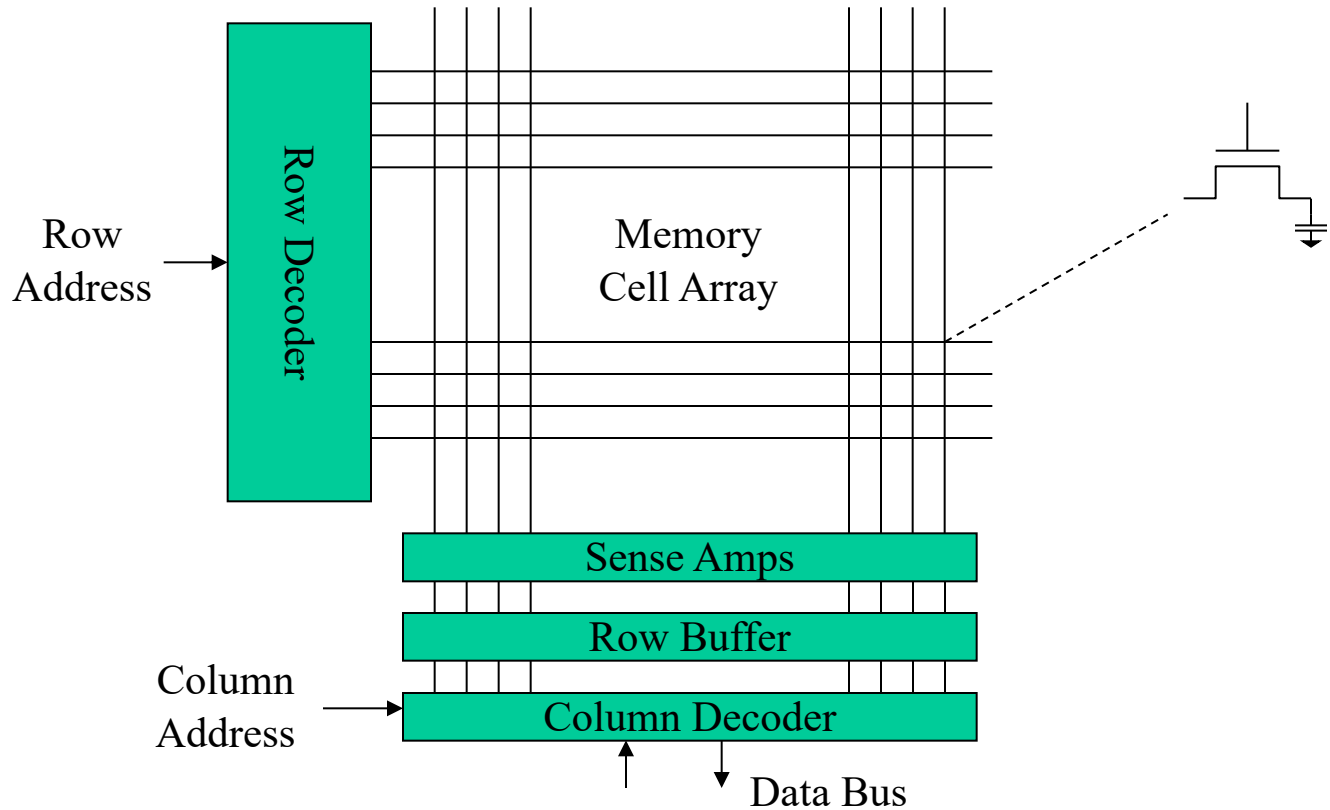

Adapted from Prof. M. Prvulovic CS 4290/6290 notes at Georgia Tech


Destructive Read

 - Bitline is precharged to $V_{dd}/2$ (versus V_{dd} in SRAM)



Charge sharing
between cell
capacitance and BL
capacitance:
*enables the readout
but destroys the
stored value*

 
After read of 0 or 1, cell contains
something close to 1/2



Adapted from Prof. M. Prvulovic CS 4290/6290 notes at Georgia Tech

Refresh / Write

 - ❑ So after a read, the contents of the DRAM cell are gone
- ❑ The values are stored in the row buffer
- ❑ **Refresh**: write them back into the cells for the next read in the future
- ❑ **Write**: modify some bits in the row buffer and write back



Adapted from Prof. M. Prvulovic CS 4290/6290 notes at Georgia Tech

DRAM vs. SRAM (2)

❑ Differences vs SRAM

- reads are *destructive*: contents are erased during reading
 - row buffer
- read lots of bits all at once, and then parcel them out based on different column addresses
 - similar to reading a full cache line, but only accessing one word at a time
- “Fast-Page Mode” FPM DRAM organizes the DRAM row to contain bits for a complete page
 - row address held constant, and then fast read from different locations from the same page

Adapted from Prof. M. Prvulovic CS 4290/6290 notes at Georgia Tech

Read-Only Memories

- ❑ Read-Only Memories are nonvolatile
 - Retain their contents when power is removed
- ❑ Mask-programmed ROMs use one transistor per bit
 - Presence or absence determines 1 or 0
- ❑ Two key architectures
 - NOR ROM
 - NAND ROM

NOR ROM Example

❑ 4-word x 6-bit ROM



- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: 010101

Word 1: 011001

Word 2: 100101

Word 3: 101010

  

Looks like 6 4-input pseudo-nMOS NORs

NAND ROM Example

❑ 4-word x 6-bit ROM


- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: 010101

Word 1: 011001


Word 2: 100101

Word 3: 101010

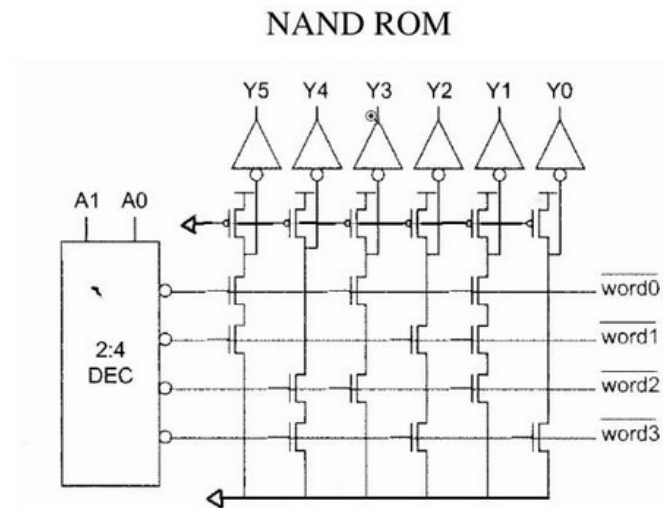


Weste/Harris F11.41

Looks like 6 4-input pseudo-nMOS NANDs

 


ROM Array Layout (NOR)

 - Unit cell is $12 \times 8 \lambda$ (about 1/10 size of SRAM)




PROMs and EPROMs

 - ❑ Programmable ROMs
 - Build array with transistors at every site
 - Burn out fuses to disable unwanted transistors
- ❑ Electrically Programmable ROMs
 - Use floating gate to turn off unwanted transistors
 - EPROM, EEPROM, Flash




Flash Programming

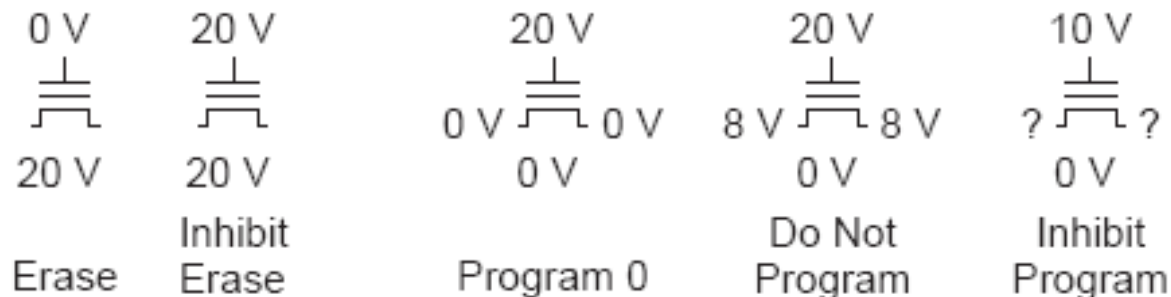- ❑ Charge on floating gate determines V_t
- ❑ Logic 1: negative V_t
- ❑ Logic 0: positive V_t
- ❑ Cells erased to 1 by applying a high body voltage so that electrons tunnel off floating gate into substrate
- ❑ Programmed to 0 by applying high gate voltage



NAND Flash

 

- ❑ High density, low cost / bit
 - Programmed one page at a time
 - Erased one block at a time
- ❑ Example:
 - 4096-bit pages
 - 16 pages / 8 KB block
 - Many blocks / memory



64 Gb NAND Flash

- ❑ 64K cells / page
- ❑ 4 bits / cell (multiple V_t)
- ❑ 64 cells / string
 - 256 pages / block
- ❑ 2K blocks / plane
- ❑ 2 planes




[Trinh09]

Semiconductor Memories

  

Wikipedia

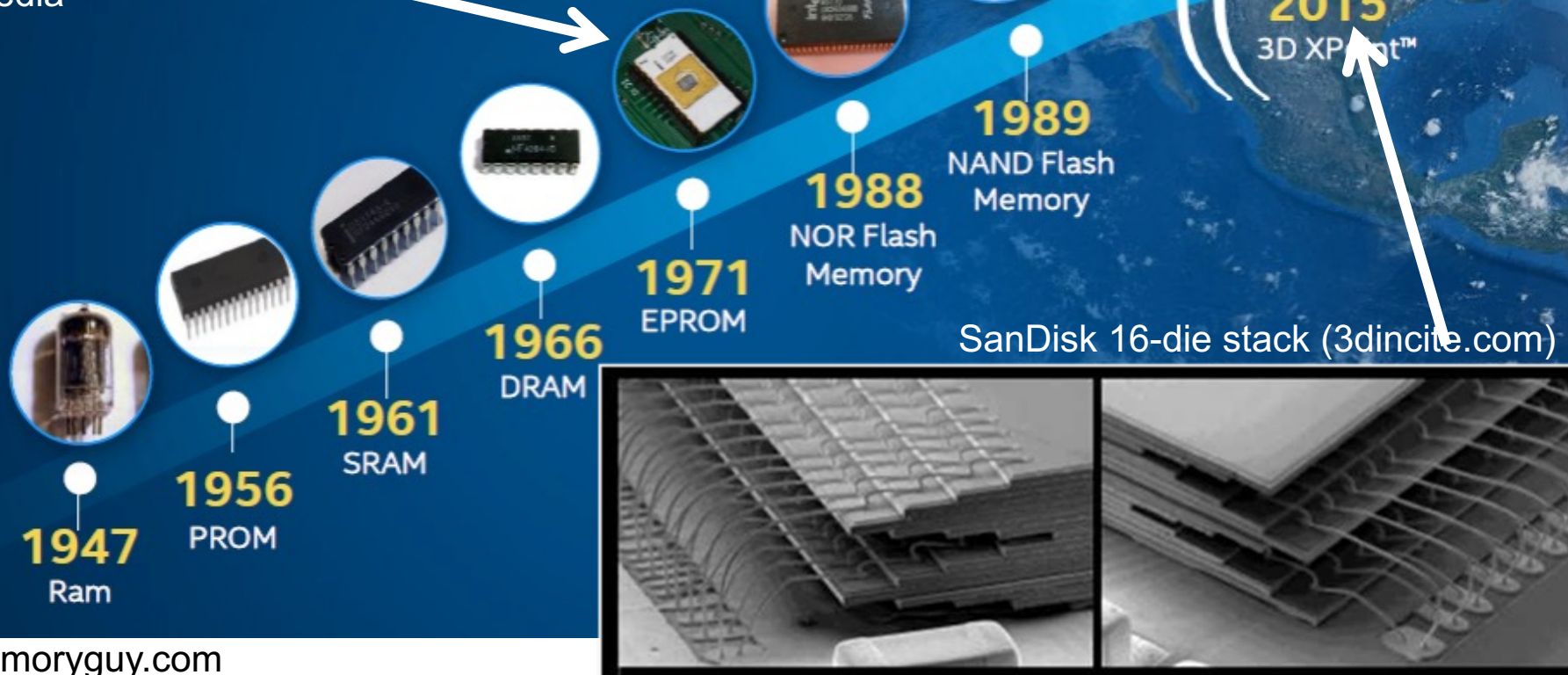


Serial Access Memories

- ❑ Serial access memories do not use an address
 - Shift Registers
 - Tapped Delay Lines
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Queues (FIFO, LIFO)


Shift Register

 - ❑ *Shift registers* store and delay data
- ❑ Simple design: cascade of registers
 - Watch your hold times!




Denser Shift Registers

 - ❑ Flip-flops aren't very area-efficient
- ❑ For large shift registers, keep data in SRAM instead
- ❑ Move read/write pointers to RAM rather than data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle




Tapped Delay Line

 - ❑ A *tapped delay line* is a shift register with a programmable number of stages
- ❑ Set number of stages with delay controls to mux
 - Ex: 0 – 63 stages of delay




Serial In Parallel Out

 - ❑ 1-bit shift register reads in serial data
 - After N steps, presents N-bit parallel output




Parallel In Serial Out

 - ❑ Load all N bits in parallel when shift = 0
 - Then shift one bit out per cycle



Queues

 - ❑ *Queues* allow data to be read and written at different rates.
- ❑ Read and write each use their own clock, data
- ❑ Queue indicates whether it is full or empty
- ❑ Build with SRAM and read/write counters (pointers)




FIFO, LIFO Queues

- ❑ *First In First Out (FIFO)*
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer
- ❑ *Last In First Out (LIFO)*
 - Also called a *stack*
 - Use a single *stack pointer* for read and write



CAMs

 - ❑ Extension of ordinary memory (e.g. SRAM)
 - Read and write memory as usual
 - Also *match* to see which words contain a *key*
 - Used in internet routers: maps MAC address to a port



10T CAM Cell

  - Add four match transistors to 6T SRAM
 - 56 x 43 λ unit cell



CAM Cell Operation

❑ Read and write like ordinary SRAM

❑ For matching:

- Leave wordline low
- Precharge matchlines
- Place key on bitlines
- Matchlines evaluate

❑ Miss line

- Pseudo-nMOS NOR of match lines
- Goes high if no words match

